## Report of the Laboratory 04

Verify Superposition Theorem for Resistive Network

Course Title: Basic Electrical Engineering Laboratory

Course Code: CSE 124

# Submitted By

Name: Mahdi Hasan Shuvo Student ID: 251-115-030 Batch & Section: 62nd (A)

## Submitted To

Honorable Sir Moshiur Ahmed Lecturer of CSE Department Metropolitan University, Sylhet

**EXPERIMENT NO: 04** 

#### NAME OF THE EXPERIMENT:

Verification of Superposition Theorem for Resistive Network

#### **OBJECTIVE:**

- To verify superposition theorem for a given circuit.
- To understand how multiple sources influence voltage across individual elements.

#### THEORY:

The **superposition theorem** states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages (or currents) caused by each independent source acting alone.


#### Conditions to turn off sources:

- Voltage source → Replace with short circuit
- Current source → Replace with open circuit

#### **APPARATUS:**

- 2 Voltage Sources
- Connecting Wires
- Multimeter
- 3 Resistors (R1 =  $470\Omega$ , R2 =  $560\Omega$ , R3 =  $680\Omega$ )

#### **CIRCUIT DIAGRAM:**

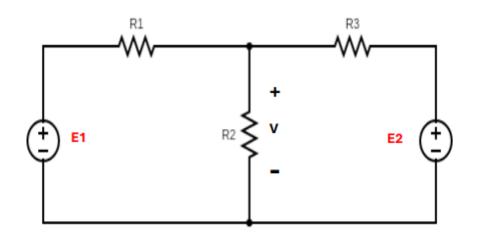

•

Number of Observation	Source Voltage (Volts)	VR2 (Volts)	V1 (Volts)	V2 (Volts)
01	E1 = 6V, E2 = 12V	5.92V	3.14V	2.78V
02	E1 = 9V, E2 = 15V	7.26V	3.89V	3.37V

## **CALCULATION:**

### **Observation 1:**

VR2 = V1 + V2= 3.14 + 2.78 = 5.92 V

### **Observation 2:**

VR2 = V1 + V2= 3.89 + 3.37 = 7.26 V

## **DISCUSSION:**

In this experiment, we applied the **superposition theorem** by analyzing the voltage across resistor R2. First, we activated both sources and recorded the total voltage across R2. Then we deactivated one source at a time (by short-circuiting voltage sources) and recorded the resulting voltages. The sum of individual voltages (V1 and V2) matched the voltage when both sources were active.

Hence, the <b>superposition theorem</b> is verified experimentally.	

Thank you, Sir.