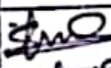
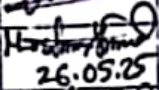
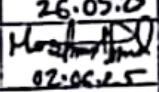


Course Code: CSE 124
 Course Title: Basic Electrical Engineering Lab
 Student Name: Salman Ahmed
 Student ID: 251-115-038
 Batch & Section: 62nd (A)

Lab Classes	Topics Covered	Date	Teacher's Signature
Lab 1	Verification of Ohm's Law	19-05-25	
Lab 2	Verification of series & parallel circuit	26-05-25	 26.05.25
Lab 3	Verification of parallel circuit	02-06-25	 02.06.25
Lab 4			
Lab 5			
Lab 6			
Lab 7			
Lab 8			
Lab 9			
Lab 10			
Lab 11			
Lab 12			
Lab 13			
Lab 14			
Lab 15			
Lab 16			

EXPERIMENT NO: 02

NAME OF THE EXPERIMENT:

VERIFICATION OF SERIES AND PARALLEL CIRCUIT

OBJECTIVE:

Our objective is to –

- Know the relationship between current & voltage for a resistor
- To know the characteristics of series & parallel resistive network

PART A – SERIES CIRCUIT

THEORY:


When resistors R1, R2, and R3 etc. are joined end to end, they are said to be connected in series. It can be proved that the equivalent resistance is equal to the sum of the three individual resistances.

In this case:


- *Current is the same through all the resistors.*
- *Different resistors have their individual voltage drops.*
- *Sum of the voltage drops is equal to the voltage applied across the three conductors.*

APPARATUS:

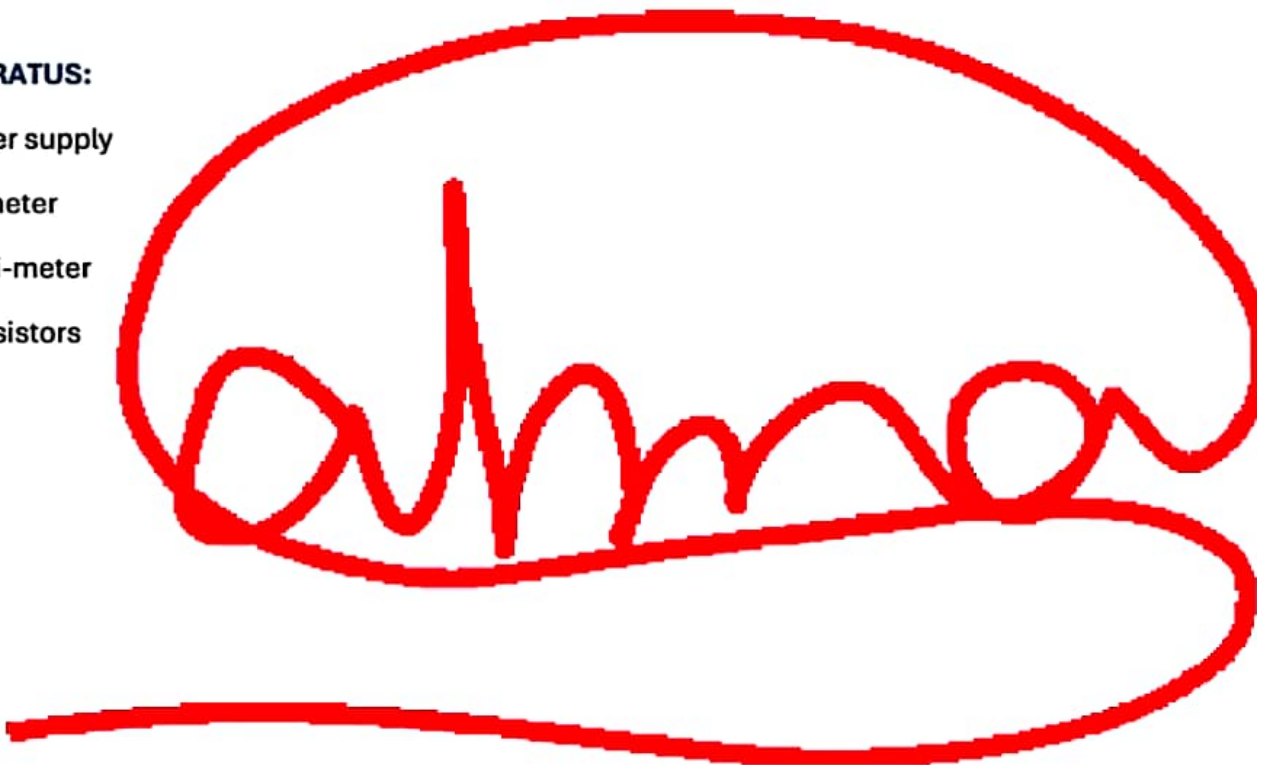- Power supply
- Ammeter
- Multi-meter
- 3 Resistors



CIRCUIT DIAGRAM:

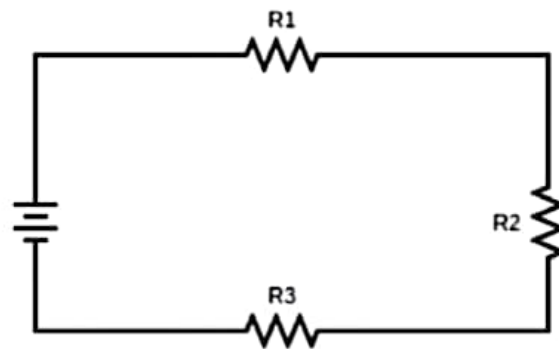

From figure, we can write equivalent resistance

$$R_{eq} = R1 + R2 + R3$$

$$\text{Circuit current, } I = V / R_{eq} = V / (R1 + R2 + R3)$$

So,

$$\text{Voltage across } R1 = V1 = I * R1 = V * R1 / R_{eq}$$

$$\text{Voltage across } R2 = V2 = I * R2 = V * R2 / R_{eq}$$

$$\text{Voltage across } R3 = V3 = I * R3 = V * R3 / R_{eq}$$

[A large, stylized red signature or scribble is present here.]

DATA TABLE:

NO. Of Observation	Supply Voltage	Resistance (Ω)			Current (mA)		Voltage (Volt)					
		R1	R2	R3	Calculated	Measured	Calculated			Measured		
							V1	V2	V3	V1	V2	V3
01	10.99	975	559	219	6.27	6.69	6.11	3	1.37	5.8	2.59	1.48
02	4.95				2.82	3.38	2.75	1.57	0.61	2.07	1.29	0.74

ahmed

DISCUSSION:

In the series circuit, the measured and calculated values are compared with the theoretical values and the behavior of the circuit is observed.

From the data, it is observed that the measured current is 6.69 mA, which is slightly higher than the calculated current of 6.27 mA. This is due to the internal resistance of the resistors and the power supply.

This part should be unique for everyone, so, its private.

Similarly, the calculated voltage across each resistor is 5.8V, 2.59V, and 1.48V. The measured voltage across each resistor is 5.8V, 2.59V, and 1.48V. The total measured voltage is 9.87V, which is slightly lower than the supply voltage of 10.99V. This is due to the internal resistance of the power supply and the connecting wires.

PART B – PARALLEL CIRCUIT

THEORY:

When resistors R1, R2, and R3 are joined as shown in fig-3, they are said to be connected in parallel.


In this case, voltages across all the resistors are same, but current in each is different.

Total current is the sum of the separate currents.

APPARATUS:

- Power supply
- Multi-meter
- 3 Resistors

CIRCUIT DIAGRAM:

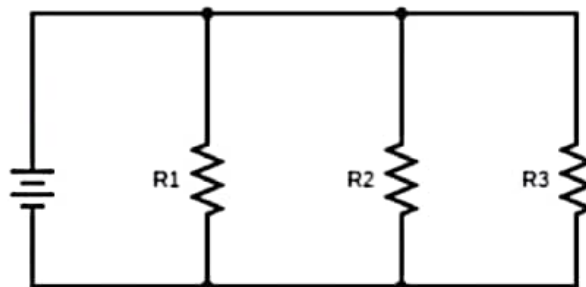

From figure, we get:

$$R_{eq} = \frac{R_1 R_2 R_3}{(R_1 R_2 + R_2 R_3 + R_1 R_3)}$$

Total current,

$$I = V / R_{eq} = V (R_1 R_2 + R_2 R_3 + R_1 R_3) / (R_1 * R_2 * R_3)$$

Current across R1 = $I_1 = I \cdot R_2 \cdot R_3 / (R_1 R_2 + R_2 R_3 + R_1 R_3)$

Current across R2 = $I_2 = I \cdot R_1 \cdot R_3 / (R_1 R_2 + R_2 R_3 + R_1 R_3)$

Current across R3 = $I_3 = I \cdot R_1 \cdot R_2 / (R_1 R_2 + R_2 R_3 + R_1 R_3)$

anna

DATA TABLE:

NO. Of Observation	Supply Voltage	Resistance (Ω)			Total Current (mA)		Branch Current (mA)					
		R1	R2	R3	Calculated	Measured	Calculated			Measured		
							I1	I2	I3	I1	I2	I3
01	4.96	2180	976	981	11.92	12.2	2.27	5.08	5.05	2.25	5.01	4.99
02	9.97				23.96	24.8	4.57	10.21	10.16	4.56	10.14	10.8

DISCUSSION:

For the parallel circuit, the branch currents and total current were observed. In the first observation, resistors of 2180 Ω , 976 Ω , and 981 Ω were used with a supply voltage of 4.96V. The calculated current for the total circuit was 11.92 mA, and the measured was 12.2 mA — a very close match. The individual branch currents were also calculated and measured.

Calculated: 5.05 mA
Measured: 5.01 mA

This part should be unique for everyone, so it's private.

These results show that in a parallel circuit, the voltage is the same across all branches, while current divides inversely with resistance.

PROBLEMS:

1. Will current be the same through resistors in a Series Circuit? What about Parallel Circuit?

Yes, current is the same through all resistors. Because there is only one path for current to flow, the same current passes through each component.

But for Parallel connection, current is divided among the branches. Each resistor gets a different amount of current depending on its resistance (Ohm's Law: $I = V/R$), but the total current is the sum of the individual branch currents.

2. Will voltage be the same across resistors in Series? What about Parallel?

No, voltage is divided across resistors in Series connection. Each resistor has a different voltage drop based on its resistance. The sum of all voltage drops equals the total supply voltage.

For Parallel connection, voltage is the same across all resistors. All branches are directly connected across the same two points, so they share the same potential difference (voltage).

